


Sum of Products - Truth Table

Example

$$f = ABC\bar{C} + \bar{B}\bar{C} + C$$

$$(A+B+\bar{C})(\bar{B}+C)(\bar{C}+C)$$


	A	B	C	F
010	0	0	0	1
	0	0	1	1
$\bar{B}=0$	0	1	0	1
$C=0$	0	1	1	1
$A=1 \text{ or } 0$	1	0	0	1
$\therefore 000$	1	0	1	1
100	1	1	0	0
	1	1	1	1

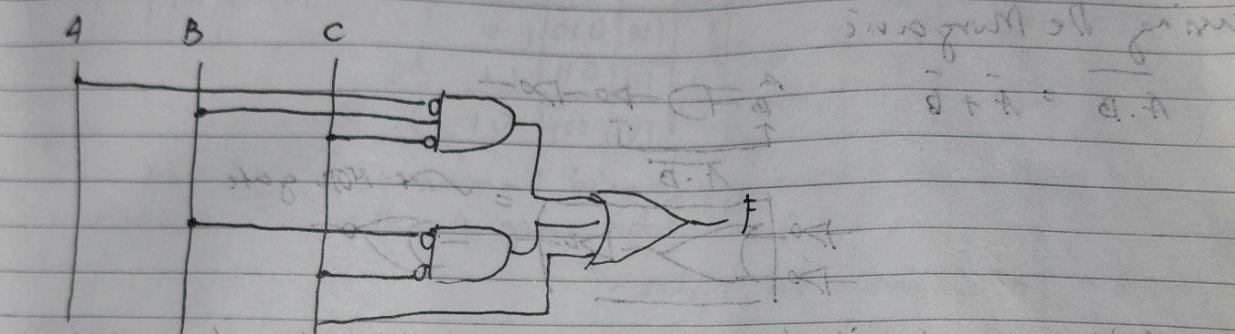

Using DeMorgan's Theorem.



$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

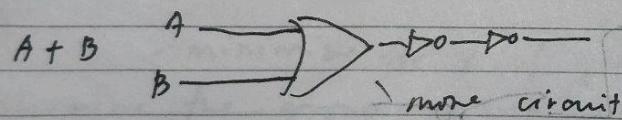
$$\overline{A + B} = \overline{A} \cdot \overline{B}$$



- An OR gate by itself is the same as an AND gate w/ inverted inputs & outputs


Updated circuit using NAND gate

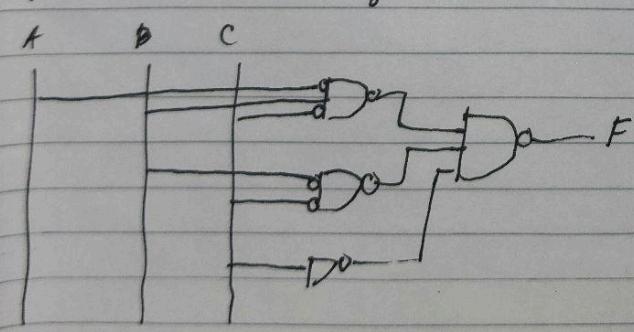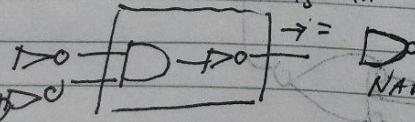

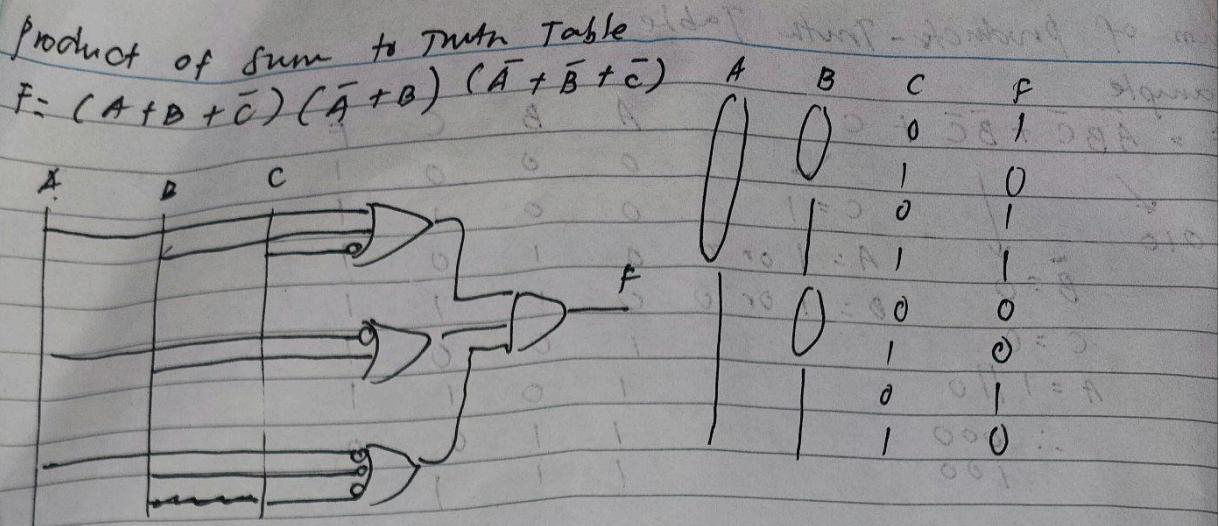

using De Morgan's

$$A \cdot B = \bar{A} + \bar{B}$$

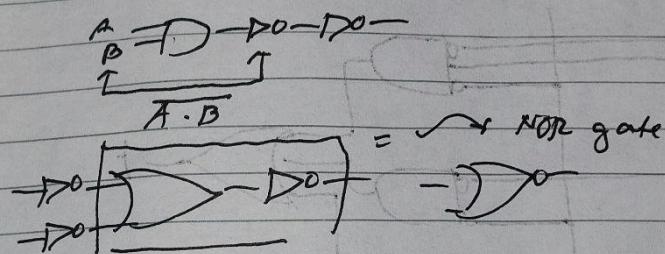


An AND gate by itself is the same as an OR gate w/ inverted inputs & outputs

Updated circuit using NOR gate

A B C

$$\overline{A} + \overline{B} = \overline{A \cdot B}$$
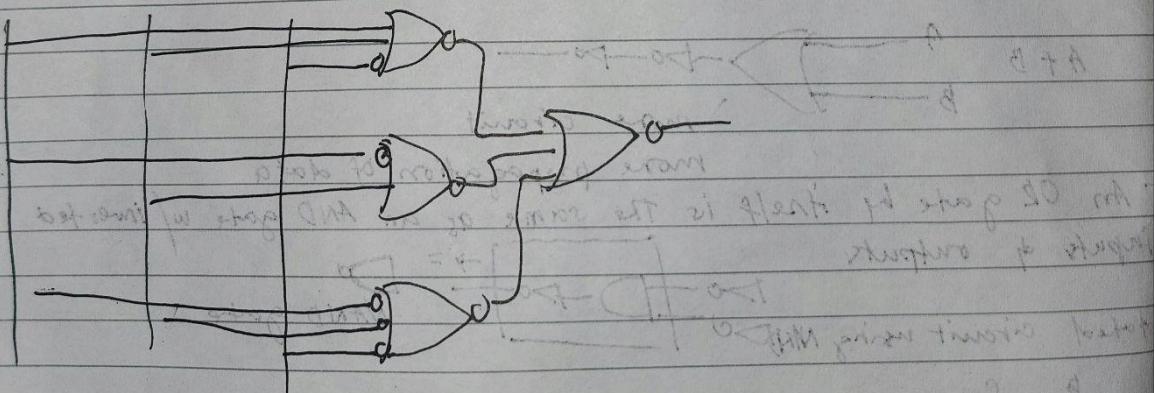
$$\overline{B \cdot A} = \overline{B} + \overline{A}$$




Karnaugh Maps (KMaps)

- used for minimizing Boolean expressions
- minimized expression
- fewer gates
- simpler circuits
- less complex circuits
- lower cost of implementation

2 Variable

	B	0	1
A	00	01	
0	10	11	
1	00	10	

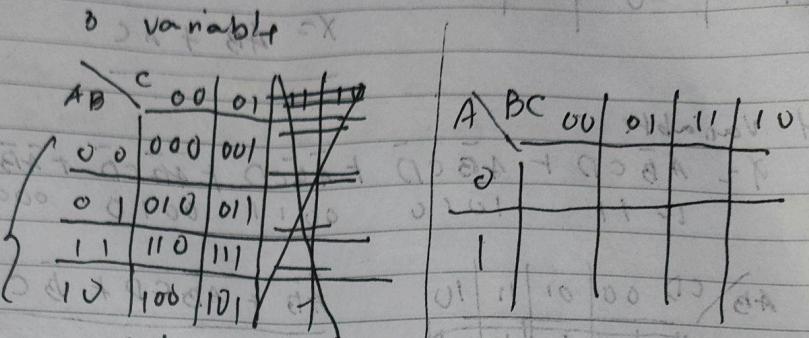

- cannot be in normal binary sequence
- must be written in Gray code

→ only 1 bit changes at a time

Tip 8

1. group the 1's (SOP) or 0's (POS)
 - maximize the group sizes - size 1 or 2ⁿ (1, 2, 4, 8, 16...)
 - select the largest group
 - minimize the # of groups by overlapping
2. determine the group product/sum expression
3. sum/product the groups

$$Y = ABC + A\bar{B}C + A\bar{B}\bar{C}$$

110 111 101

First group

(2001) 2nd group

$A\bar{B}$	C	0	1
00	0	0	0
01	0	0	0
11	1	1	1
10	0	1	1

$$Y = AB + AC$$

4 variable

$$Y = \bar{A}\bar{B}CD + A\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + A\bar{B}CD + A\bar{B}C\bar{D}$$

$A\bar{B}$	CD	00	01	11	10
00	0	0	1	1	1
01	0	0	0	0	0
11	0	0	1	0	0
10	0	1	1	1	1

$$\bar{A}\bar{B} + A\bar{B}CD + \bar{B}C = F$$

$A\bar{B}$	CD	00	01	11	10
00	0	0	1	1	1
01	0	0	1	1	1
11	0	1	1	1	1
10	1	1	1	1	1

$$\bar{A}\bar{B} + \bar{B}C + D = F$$

$\bar{B}A$	00	01	11	10
00	0	0	1	1
01	0	0	1	1
10	1	1	1	1
11	1	1	1	1
10	1	1	1	1

$$\bar{B}A + D + C\bar{B}\bar{D} = F$$

using Product of Sums

wx	yz	00	01	11	10	
00	00	0	0	0	0	
01	00	0	0	0	0	
11	00	0	0	0	0	
10	00	0	0	0	0	

$\rightarrow (W + Y)$

wx	yz	00	01	11	10	
00	00	0	0	0	0	
01	00	0	0	0	0	
11	00	0	0	0	0	
10	00	0	0	0	0	

$\rightarrow (W + Y')(Y + Z)$

Don't care conditions

$$f(A, B, C, D) = \sum m(0, 1, 4, 5, 6, 10, 11, 13) + d(2, 3)$$

\times

AB	CD	00	01	11	10	
00	00	1	1	X	X	
01	00	1	1	1	1	
11	00	1	1	1	1	
10	00	1	1	1	1	

$\rightarrow A'CD + A'CB + A'CA + A'CB' = (A' + B)(C + D)$

θ

variable kmap

$$f(A, B, C, D, E) = \sum(0, 1, 6, 7, 8, 9, 21, 22, 23, 29, 31)$$

		A=0	
		A=1	
BC		DE	
00	01	11	10
00	1	3	2
01	4	5	7
11	12	13	15
10	8	9	11

BC		DE		
00		01	11	10
00	16	17	19	18
01	20	21	23	22
11	28	11	29	31
10	24	25	27	26

$\bar{A}C\bar{D}$

$$f(A, B, C, D, E) = \underline{\bar{A}\bar{C}\bar{D} + ACE + \bar{B}CD}$$

$$f(A, B, C, D, E) = \sum_m(0, 16) + \sum_d(17, 18, 19, 20, 21, 22, 23)$$

BC		DE	
00		01	11
00	1	1	3
01	4	5	7
11	12	13	15
10	8	9	11


BC		DE	
00		01	11
00	1	16	17
01	x	20	21
11	28	29	31
10	24	25	27

$$f(A, B, C, D, E) = \underline{\bar{B}\bar{C}\bar{D}\bar{E} + A\bar{B}}$$

Using NAND & NOR as Universal gates

NAND - all inputs are the same
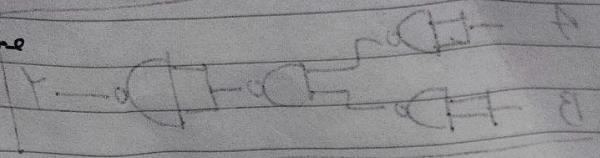
$$Y = \overline{A \cdot A} = \overline{A}$$




As NOT gate

- all inputs are the same


$$Y = \overline{A} = \overline{A \cdot A}$$

$$\boxed{\begin{array}{c} A \rightarrow D_o \rightarrow Y \\ A \rightarrow D_o \end{array}} = A \rightarrow D_o \rightarrow Y$$

$$A = Y$$

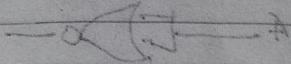

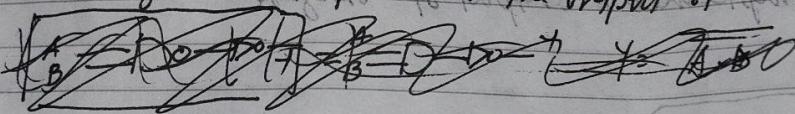As AND gate - complement the output of NAND gate



- use the NAND NOT gate to complement the NAND gate

$$\overline{D_o \cdot D_o} \rightarrow Y = \overline{\overline{A \cdot B}}$$

$$\boxed{\begin{array}{c} A \rightarrow D_o \rightarrow D_o \rightarrow Y \\ B \rightarrow D_o \end{array}} = A \cdot B$$

As an OR gate - use the NAND NOT gate to complement inputs

$$Y = \overline{A \cdot B} = \overline{\overline{A} + \overline{B}}$$


$$Or = A + B$$

$$\begin{array}{c} A \rightarrow D_o \rightarrow Y = (\overline{A \cdot B}) \\ B \rightarrow D_o \end{array}$$

$$= A + B$$

$$\boxed{\begin{array}{c} A \rightarrow D_o \rightarrow D_o \rightarrow + \\ B \rightarrow D_o \end{array}}$$

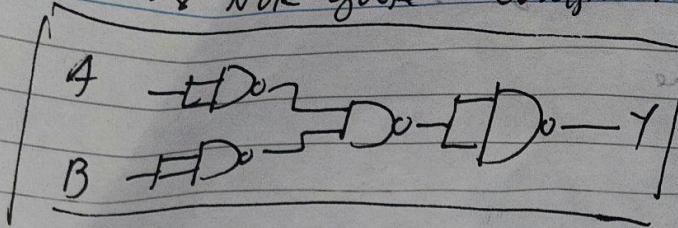
NAND as NOR gate - complement the output of OR gate



NOR as universal gate


As NOT gate

$$Y = \overline{A}$$

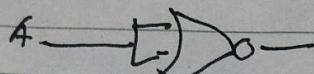


As OR gate - complement output of NOR gate

$$\overline{B} = D \rightarrow D_0$$

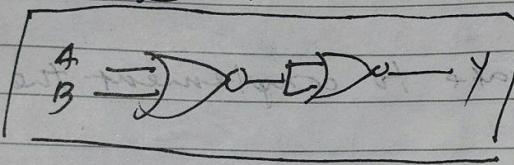


As AND gate $Y = \overline{A+B} = \overline{A} \cdot \overline{B}$

- complement the inputs NOR gate

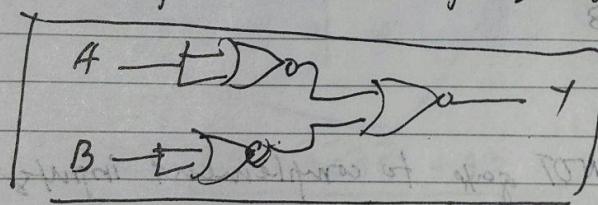

As NAND gate

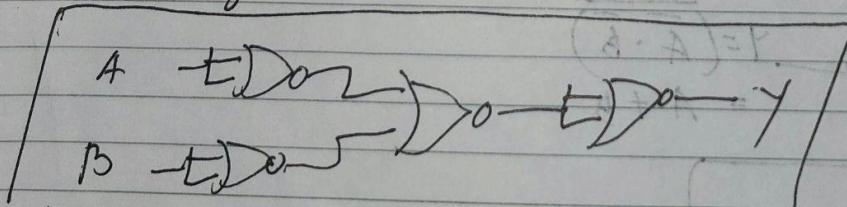

Tabular Method (Quine-McCluskey Minimization)

1. Prime Implicant

2. Essential Prime Implicant

- Implicant (group of 1s)

- Prime Implicant (largest group of 1s)

- Essential Prime Implicant (Prime Implicant having at least 1 minterm that can't be combined)


$$F(A, B, C, D) = \sum_m(0, 1, 3, 7, 8, 9, 11, 15)$$

1. group the minterms by their number of 1s

Grp #	Minterm	Binary Value	A	B	C	D
0	m_0	0 0 0 0	0	0	0	0
1	m_1	0 0 0 1	0	0	0	1
	m_8	1 0 0 0	1	0	0	0
2	m_3	0 0 1 1	0	0	1	1
	m_9	1 0 0 1	1	0	0	1
3	m_7	0 1 1 1	0	1	1	1
	m_{11}	1 0 1 1	1	0	1	1
4	m_{15}	1 1 1 1	1	1	1	1

Group #	Matching pair	Binary Value	ABCD
0	m_0, m_1	0 0 0 -	twice
	m_0, m_8	- 0 0 0	indipendent string
1	m_1, m_3	0 0 + 1	(to group) twice
	m_1, m_9	- 0 0 1	(to group) twice
	m_8, m_9	1 0 0 -	twice to win
2	(m_3, m_7)	0 - 1 1	3.1
	m_3, m_{11}	- 0 1 1	$(2-101181F, 1, 0) \oplus 3 = 0$
	m_7, m_{11}	1 0 - 1	
3	m_7, m_{15}	- 1 1 1	to reduce size of sum
	m_{11}, m_{15}	1 - 1 1	maximal
0	m_0, m_1, m_8, m_9	- 0 0 -	BC
	m_0, m_1, m_8, m_9	- 0 0 -	
	m_1, m_3, m_9, m_{11}	1 0 0 0	
1	m_1, m_3, m_9, m_{11}	- 0 - 1	BD
	m_1, m_9, m_3, m_{11}	- 0 - 1 1	
		1 0 0 1	
2	m_3, m_7, m_{11}, m_{15}	- - 1 1	CD
	m_3, m_{11}, m_7, m_{15}	- - 1 1	
		1 1 0 1	
Prime Implicant Table			
P.I.	minterms	0 1 3 7 8 9 11 15	
$\bar{B}C$	0, 1, 8, 9	(✓) ✓	✓ ✓
$\bar{B}D$	1, 3, 9, 11	✓ ✓	✓ ✓
CD	3, 7, 11, 15	✓ (✓)	✓ (✓)

Verify w/ KMap

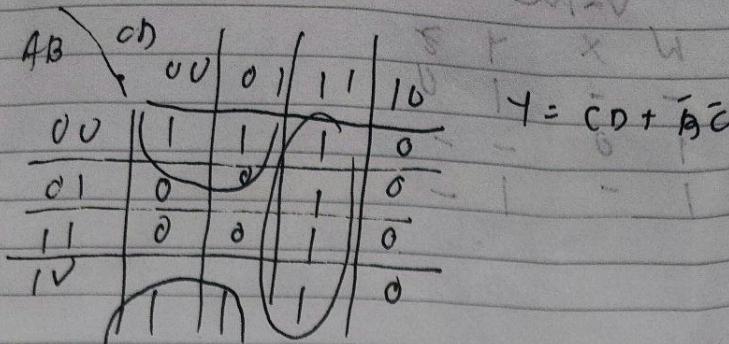

$$Y = \overline{CD} + \overline{B}\bar{C}$$

Example 2 $F(W, X, Y, Z) = \sum_m(2, 6, 8, 9, 10, 11, 14, 15)$

Grp # Minterm Delegation | Binary Variable

		W	X	Y	Z
0	2	0	0	1	0
	8	1	0	0	0
1	6	0	1	1	0
	9	1	0	0	1
	10	1	0	1	0
2	11	1	0	1	1
	14	1	1	1	0
4	15	1	1	1	1
<u>Grp</u>	<u>8</u>				
0	2, 6	0	-	1	0
	2, 10	-	0	1	0
	8, 9	1	0	0	-
	8, 10	1	0	-	0
1	6, 14	-	1	1	0
	9, 11	1	0	-	1
	10, 11	1	0	1	-
	10, 14	1	-	1	0
2	11, 15	1	-	1	1
	14, 15	1	1	1	-
<u>0</u>	<u>2, 6, 10, 14</u>	-	-	1	0
	<u>2, 10, 6, 14</u>	1	-	1	0
	<u>8, 9, 10, 11</u>	0	-	-	-
	<u>8, 10, 9, 11</u>	1	0	-	-
1	<u>10, 11, 14, 15</u>	1	-	1	-
	<u>10, 14, 11, 15</u>	1	-	1	-

Grp #	Min Term Prolagation	Binary Value	Sum of U
0	2, 6, 10, 14 8, 9, 10, 11	$\bar{w}\bar{x} + \bar{w}\bar{y} = 1$ 0 0 - -	0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0
1	10, 11, 14, 15	1 - 1 -	1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1
			0 1 0 1 0 1 0 1 0 1 0 1 0 1 0 1

Prime Implicant Table

P1	P2	P6	P8	P9	P10	P11	P14	P15
$w\bar{x}$	$(\bar{w}, \bar{v}, \bar{u}, \bar{w})$	$\bar{w}\bar{v}$	$\bar{w}\bar{u}$	$\bar{w}\bar{v}\bar{u}$	$\bar{w}\bar{v}\bar{u}\bar{w}$	$\bar{w}\bar{v}\bar{u}\bar{w}$	$\bar{w}\bar{v}\bar{u}\bar{w}$	$\bar{w}\bar{v}\bar{u}\bar{w}$
wx	(w, v, u, w)	wv	wu	wvu	$wvuw$	$wvuw$	$wvuw$	$wvuw$
wy	(w, v, u, y)	wv	wu	wvu	$wvuw$	$wvuw$	$wvuw$	$wvuw$